



中国科学院大学

University of Chinese Academy of Sciences

CS101

Systems Thinking

Modularization-1:

Combinational Circuits and Sequential Circuits

zxu@ict.ac.cn

zhangjialin@ict.ac.cn

Outline

- What is systems thinking?
- Three objectives of systems thinking
- Abstraction
- Modularization
 - Modularization and modules
 - Combinational circuits
 - Logic gates and combinational circuits
 - The information hiding principle
 - Adders
 - An adder-subtractor controlled by multiplexers
 - Sequential circuits
 - Types of memory cells and the D flip-flop
 - General organization of sequential circuit
 - A serial adder example
 - Instruction Set and Instruction Pipeline
 - Software Stack
- Seamless transition

These slides acknowledge sources for additional data not cited in the textbook


4.1 Modularization and modules

- Modularization is a systems thinking method, similar to divide-and-conquer in algorithmic thinking
 - Divide a system into multiple subsystems called modules
 - Compose modules into a system (higher-level abstraction)
- In a system with modularization
 - Two modules may be **interconnected**, but normally **do not overlap**
- Modularization is a special form of abstraction where the information hiding principle is followed
- Modularization, i.e., how to divide and compose a system, is an art, needing human imagination and creativity
- Understand how modularization works via a design journey
 - of higher and higher hardware subsystem abstractions
 - from designing **gates** to designing an **instruction pipeline**

4.1.1 Logic gates and combinational circuit


- Logic gates: electronic circuits realizing Boolean operators

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

 


AND

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

 

OR

X	Z
0	1
1	0

 


NOT

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0




XOR

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

 

NAND

circle means NOT

 


CMOS circuit for NAND

4.2.1 Logic gates and combinational circuit


- Logic gates: electronic circuits realizing Boolean operators

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

 


AND

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

 

OR

X	Z
0	1
1	0

 


NOT

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0




XOR

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

 



NAND

 

CMOS circuit for NAND

circle means NOT


$$Z = \overline{(X \cdot Y)} \cdot W$$

  


4.2.1 Logic gates and combinational circuit

- Logic gates: electronic circuits realizing Boolean operators


X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

 



X	Z
0	1
1	0

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0



X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

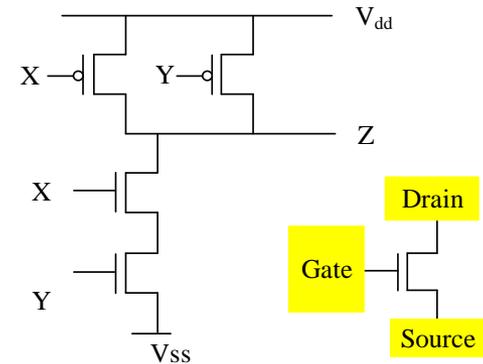 



CMOS circuit for NAND

Vss: ground (0); Vdd: high voltage (1)

- A combinational circuit is comprised of interconnected gates without feedback wires

- Any combinational circuit has a corresponding **Boolean expression**
- Any Boolean expression has a corresponding combinational circuit
- A combinational circuit can be shown as a **logic diagram**

$$Z = \overline{(X \cdot Y)} \cdot W$$

  


CMOS circuit

4.2.1 Logic gates and combinational circuit

- Logic gates: electronic circuits realizing Boolean operators

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

 


AND

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1



OR

X	Z
0	1
1	0

 


NOT

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0




XOR

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

 

NAND

 


CMOS circuit for NAND


A combinational circuit is comprised of interconnected gates without feedback wires

- Any combinational circuit has a corresponding Boolean expression
- Any Boolean expression has a corresponding combinational circuit
- A combinational circuit can be shown as a logic diagram
 
$$Z = \overline{\overline{X \cdot Y}} \cdot W$$



Such feedback wire is not allowed

 


CMOS circuit

 4.2.2 The information hiding principle

- A module only exposes its interface and visible behaviors, but hides internal details and internal behavior
- Three types of abstractions are shown of the same combinational circuit


- Boolean expression
- Logic diagram
- CMOS circuit



- The three yellow areas are different abstractions for the same thing
 - a 2-input-1-output NAND gate
- The Boolean expression and the logic diagram abstractions hide internal details of the CMOS implementation
- The former two are simpler and allow different implementations

 4.2.3 Adders


- Add two unsigned numbers X and Y to generate result sum Z
 - Consider the carry-in bit C_{in} and the carry-out bit C_{out}
 - Use the same algorithm we use when doing addition by pen and paper
- For one bit, design a **full adder**
 - Here, “full” means the adder considers carry-in and carry-out bits
 - **1-minute quiz:** given X , Y and C_{in} , what are the expressions of Z and C_{out} ?



Full adder symbol

Full adder


- Add two unsigned numbers X and Y to generate result sum Z
 - Consider the carry-in bit C_{in} and the carry-out bit C_{out}
 - Use the same algorithm we use when doing addition by pen and paper
- For one bit, design a full adder
 - Here, “full” means the adder considers carry-in and carry-out bits
 - **1-minute quiz:** given X , Y and C_{in} , what are the expressions of Z and C_{out} ?
 - A: Derive the truth table from the manual addition method
Then, derive the Boolean expressions for Z and C_{out}
 - $Z = X \oplus Y \oplus C_{in}$
 - $C_{out} = (X \cdot Y) + (X \oplus Y) \cdot C_{in}$

 

Full adder symbol

C _{in}	X	Y	Z	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Truth table

 


Implementation by gates

Ripple-carry adder


- Add two unsigned numbers X and Y to generate result sum Z
 - Consider the carry-in bit C_{in} and the carry-out bit C_{out}
 - Use the same algorithm we use when doing addition by pen and paper
- For n -bit, design an n -bit **ripple-carry adder** (assuming $n=4$ in example)
 - Use $X+Y=1011+1001 = 10100$ to verify that the 4-bit adder works correctly
 - **1-minute quiz:** How much time to do the addition? Use gate delay as the unit

 

Full adder symbol

 

Its implementation by gates

 


A 4-bit ripple-carry adder


Ripple-carry adder

- Add two unsigned numbers X and Y to generate result sum Z
 - Consider the carry-in bit C_{in} and the carry-out bit C_{out}
 - Use the same algorithm we use when doing addition by pen and paper
- For n -bit, design an n -bit **ripple-carry adder** (assuming $n=4$ in example)
 - **1-minute quiz:** How much time to do the addition? Use gate delay as the unit
 - Answer 1: total delay $\sim 3n$; about 12 gate delays when $n=4$
 - Because each full adder needs 3 gate delays to generate carry-out


- Is this answer correct?

 

Full adder symbol

 


Its implementation by gates

 

A 4-bit ripple-carry adder

Ripple-carry adder



- Add two unsigned numbers X and Y to generate result sum Z
 - Consider the carry-in bit C_{in} and the carry-out bit C_{out}
 - Use the same algorithm we use when doing addition by pen and paper
- For n -bit, design an n -bit **ripple-carry adder** (assuming $n=4$ in example)
 - **1-minute quiz:** How much time to do the addition? Use gate delay as the unit
 - Answer 2: $2n+1$. 9 gate delays for $n=4$
 - Only C_1 needs 3 gate delays, and another C_i needs only 2 additional gate delays.
 - Why? Because for $1 \leq i < n$, $X_i \oplus Y_i$ is already generated when C_1 becomes available
 - Red line shows the longest path

 

Expand to show the gate-level details

A much faster adder

- Instead of compute the carry bits one by one in n steps, we can compute all the n carry bits **in parallel** in one step
 - This step needs 3 gate delays
- Afterwards, the n sum bits are computed in parallel in one step
 - This step needs 1 gate delay
- 4 gate delays in total
 - Compared to $2n - 1$ gate delays for ripple-carry adder
- Constrained by **fan-in** and **fan-out** in practice
 - A gate can only safely receive a few inputs
 - A gate output cannot drive too many wires

  


4.2.4 A combinational circuit can compute multiple functions via selection by control signals

- An adder-subtractor controlled by a **multiplexer** (MUX in short)
 - Control signal S to select addition (S=0) or subtraction (S=1)
 - Subtraction is adding negative, e.g., $5-5 = 5+(-5)$
 - The negative value of a number X is the two's complement of X
 - Let $X = Y = 5$, i.e., $X_3X_2X_1X_0 = Y_3Y_2Y_1Y_0 = 0101$
 - Then, $X - Y = 5 + (-5) = 5 + \text{Two's complement of } 5$

$$\begin{aligned} &\rightarrow 0101 + (\overline{0101} + 0001) \\ &= 0101 + 1011 \\ &= 10000 = C_4 Z_3 Z_2 Z_1 Z_0 \end{aligned}$$


$$Z = \begin{cases} X & \text{if } S = 0 \\ Y & \text{if } S = 1 \end{cases}$$

S	X	Y	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 


S	Z
0	X
1	Y

A multiplexer

 

A two's complement 4-bit adder

 


and an adder-subtractor

4.3 Sequential circuits


- **Sequential circuit = combinational circuit + state circuit**
 - With states, a system can execute multi-step computational processes
 - Each step computes two types of values
 - The current output values
 - The next state values
 - Both are computed from
 - The current input values
 - The current state values
- **Correspondences to abstractions in logic thinking**
 - A combinational circuit is equivalent to a Boolean expression
 - A sequential circuit is equivalent to an automaton
- **States in hardware circuits are implemented by two types of basic circuits**
 - Memory cells
 - flip-flops: logic circuits with feedback wires
 - We discuss only the D flip-flop

 4.3.1 Types of memory technology

- Non-volatile memory (NVM): content is retained when power is off
 - ROM (read-only memory)
 - Read-write NVM
- Volatile memory: content is lost when power is off
 - DRAM (dynamic random access memory)
 - Simple and inexpensive
 - Needs to constantly refresh its content (once every 7.8-128 μ s)
 - Because the capacitor leaks electricity after charging
 - SRAM (static random access memory)
 - More complex but avoid refreshing overhead
 - Faster but more expensive than DRAM



DRAM cell
1 transistor and
1 capacitor

 

SRAM cell
6 transistors


Type	Latency	Price \$/GB
Register	100s ps	N/A
SRAM	100s ps ~ 10 ns	\$100's ~1000s /GB
DRAM	10s ~ 100 ns	\$2~4 /GB
NVM: Main Memory	100 ns ~ 10 μ s	\$6 / GB
NVM: SSD	10 μ s ~ 1 ms	\$0.1~0.2 / GB
Hard Disk: HDD	> A few ms	\$0.02 / GB

4.3.2 D flip-flop


- We can also use gates to form state circuits
 - With feedback wires
- A common type is the **delay flip-flop**, or D flip-flop
 - 2-input-2-output, where the 2 states (outputs) are negation of each other
 - Input D is data input; Input E (enable signal) is often the clock signal CLK
 - Functionality: when enabled, Q is D delayed one clock cycle
 - When E=0, Q remains the same; when E=1, the new Q will be the current D

E	D	Q	Q _{next}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

D flip-flop: Truth table

 

Internal logic diagram

 



Symbol

4.3.2 D flip-flop


- A common type is the **delay flip-flop**, or D flip-flop
 - 2-input-2-output, where the 2 states (outputs) are negation of each other
 - Input D is data input; Input E (enable signal) is often the clock signal CLK
 - Functionality: when enabled, Q is D delayed one clock cycle

E	D	Q	Q _{next}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

D flip-flop: Truth table

  


Internal logic diagram

 

Symbol

 
4.3.3 General organization of sequential circuits

- Any sequential circuit can be organized as shown below
 - Comprised of two combinational circuits and a state circuit
 - Driven by a clock signal CLK
 - The state circuit consists of one or more D flip-flops
 - The output circuit F: $Out(t) = F(In(t), State(t))$
 - The next-state circuit G: $State(t+1) = G(In(t), State(t))$
- This is the logic diagram for a sequential circuit
 - Also called synchronous sequential circuit
 - Because the sequential circuit is synchronized by the clock signal



 4.3.3 General organization of sequential circuits

- Any sequential circuit can be organized as shown below
 - Comprised of two combinational circuits and a state circuit
 - Driven by a clock signal CLK
 - The state circuit consists of one or more D flip-flops
 - The output circuit F: $\text{Out}(t) = F(\text{In}(t), \text{State}(t))$
 - The next-state circuit G: $\text{State}(t+1) = G(\text{In}(t), \text{State}(t))$
- An input or output may have multiple bits




We will go through the process of designing a 4-bit serial adder

4.3.4 Design a 4-bit serial adder

- To perform $Z_3Z_2Z_1Z_0 = X_3X_2X_1X_0 + Y_3Y_2Y_1Y_0$ in 4 steps
 - Each step performs a full addition
- First, **design** the adder
- Second, **verify** the correctness of the adder
- Use of an example is helpful in both design and verification
 - $X + Y = 11_{10} + 9_{10}$
 $= 1011_2 + 1001_2 = 10100_2$
 $= 20_{10} = 4_{10}$ and overflow
 $= 0100_2$ and overflow
 - Therefore, $Z_3Z_2Z_1Z_0 = 0100$ and the carry-bit $C_4 = 1$

Design process


- Perform $Z_3Z_2Z_1Z_0 = X_3X_2X_1X_0 + Y_3Y_2Y_1Y_0$ in 4 steps
 - Example: $X + Y = 11_{10} + 9_{10} = 1011_2 + 1001_2 = \mathbf{10100}_2 = 20_{10} = "4_{10} \text{ and overflow}"$
- Design process
 1. Q: how many bits (or D flip-flops) are needed for the state circuit?
 - A: 1 bit to hold the carry bit. Only one D flip-flop is needed. Denote the state as Q.
 2. Draw the logic diagram for the sequential circuit
 - How?
 - Some students directly draw it by applying the principle of serial addition
 - Those students can skip the next 5 slides
 - Some prefer to understand behavior of the sequential circuit (the figure below) by executing $X + Y$ (serial addition) using the paper+pencil method

 

Design process

- Perform $Z_3Z_2Z_1Z_0 = X_3X_2X_1X_0 + Y_3Y_2Y_1Y_0$ in 4 steps
 - Each step is a clock cycle
 - Each step performs a full addition
- Use the paper+pencil method
 - Step 1 (clock cycle 1) is shown in bold. Note that initial state $Q(0) = C_0 = 0$
 - Given $C_0 = 0, X_0 = 1, Y_0 = 1$, circuits F, G should output $Z_0 = 0, C_1 = Q(1) = 1$

 
$$\begin{array}{r}
 101\mathbf{1} = X \\
 + 100\mathbf{1} = Y \\
 \hline
 0 = C \\
 0 = Z
 \end{array}$$



Design process

- Perform $Z_3Z_2Z_1Z_0 = X_3X_2X_1X_0 + Y_3Y_2Y_1Y_0$ in 4 steps
 - Each step takes a clock cycle to complete
 - Each step performs a full addition
- Use the paper+pencil method
 - Step 1 (clock cycle 1) is shown in bold. Note that $Q(0) = C_0 = 0$
 - Given $C_0 = 0, X_0 = 1, Y_0 = 1$, circuits F, G should output $Z_0 = 0, C_1 = Q(1) = 1$
 - At the final moment of clock cycle 1 (and the beginning of cycle 2), the D flip-flop output $Q(t)$ takes the value of the D flip-flop data input $Q(t+1)$

 
$$\begin{array}{r}
 101\mathbf{1} = X \\
 + 100\mathbf{1} = Y \\
 \hline
 \mathbf{1}0 = C \\
 \mathbf{0} = Z
 \end{array}$$



Design process

- Perform $Z_3Z_2Z_1Z_0 = X_3X_2X_1X_0 + Y_3Y_2Y_1Y_0$ in 4 steps
 - Each step performs a full addition
- Use the paper+pencil method
 - Step 2 (clock cycle 1) is shown in bold. Note that $Q(1) = C_1 = 1$

 
$$\begin{array}{r}
 1011 = X \\
 + 1001 = Y \\
 \hline
 1100 = C \\
 00 = Z
 \end{array}$$



Design process



- Perform $Z_3Z_2Z_1Z_0 = X_3X_2X_1X_0 + Y_3Y_2Y_1Y_0$ in 4 steps
 - Each step performs a full addition
 - Continue to do Step 3 and 4
 
$$\begin{array}{r}
 1011 = X \\
 + 1001 = Y \\
 \hline
 10110 = C \\
 0100 = Z
 \end{array}$$



Design process

  - Draw the logic diagram for the sequential circuit
 - Derive the state-transition diagram





q_0 denotes $C=0$
 q_1 denotes $C=1$

$$\begin{array}{r}
 1\ 0\ 1\ 1 = X \\
 +\ 1\ 0\ 0\ 1 = Y \\
 \hline
 1\ 0\ 1\ 1\ 0 = C \\
 0\ 1\ 0\ 0 = Z
 \end{array}$$

Design process

  - Derive the state-transition diagram (remember that Q denotes carry C)
- Derive the truth table and Boolean expressions for F, G



q_0 denotes $C=0$
 q_1 denotes $C=1$

Q	X	Y	Z	Q_{next}
q_0	0	0	0	q_0
q_0	0	1	1	q_0
q_0	1	0	1	q_0
q_0	1	1	0	q_1
q_1	0	0	1	q_0
q_1	0	1	0	q_1
q_1	1	0	0	q_1
q_1	1	1	1	q_1

$$Z = F(X, Y, Q) = X \oplus Y \oplus C$$

$$Q_{next} = G(X, Y, Q) = (X \cdot Y) + (X \oplus Y) \cdot Q$$

Verification process

- Given $X_3X_2X_1X_0 = 1011$, $Y_3Y_2Y_1Y_0 = 1001$, $C_0 = 0$, verify the resulting sequential circuit, noting that F: $Z = X \oplus Y \oplus C$; G: $Q_{\text{next}} = (X \cdot Y) + (X \oplus Y) \cdot Q$
- Step 1:
 - $Z_0 = X_0 \oplus Y_0 \oplus C_0 = 1 \oplus 1 \oplus 0 = 0$
 - $C_1 = (X_0 \cdot Y_0) + (X_0 \oplus Y_0) \cdot C_0 = (1 \cdot 1) + (1 \oplus 1) \cdot 0 = 1$
- Step 2:
 - $Z_1 = X_1 \oplus Y_1 \oplus C_1 = 1 \oplus 0 \oplus 1 = 0$
 - $C_2 = (X_1 \cdot Y_1) + (X_1 \oplus Y_1) \cdot C_1 = (1 \cdot 0) + (1 \oplus 0) \cdot 1 = 1$
- Step 3:
 - $Z_2 = X_2 \oplus Y_2 \oplus C_2 = 0 \oplus 0 \oplus 1 = 1$
 - $C_3 = (X_2 \cdot Y_2) + (X_2 \oplus Y_2) \cdot C_2 = (0 \cdot 0) + (0 \oplus 0) \cdot 1 = 0$
- Step 4:
 - $Z_3 = X_3 \oplus Y_3 \oplus C_3 = 1 \oplus 1 \oplus 0 = 0$
 - $C_4 = (X_3 \cdot Y_3) + (X_3 \oplus Y_3) \cdot C_3 = (1 \cdot 1) + (1 \oplus 1) \cdot 0 = 1$

The final result is $Z_3Z_2Z_1Z_0 = 1011$, with $C_4 = 1$ indicating overflow

